

# AN12380

## Antenna design guide for NTAG 5 link and NTAG 5 switch

Rev. 1.1 — 30 January 2020  
580311

Application note  
COMPANY PUBLIC

### Document information

Info	Content
<b>Keywords</b>	NTAG 5 link, NTAG 5 switch, Antenna Theory, Antenna Design, Measurement Methods, Antenna Design Procedure
<b>Abstract</b>	NTAG 5 needs to be connected to an antenna to access NTAG 5 via NFC interface. This application note provides guidance for designing such antenna.



**Revision history**

<b>Rev</b>	<b>Date</b>	<b>Description</b>
1.1	20200130	Antenna matching calculation sheet added in the document
1.0	20200109	First released version

**Contact information**

For more information, please visit: <http://www.nxp.com>

## 1. Introduction

---

NTAG 5 family is ISO/IEC 15693 and NFC Forum Type 5 Tag compliant, with an EEPROM, SRAM and I<sup>2</sup>C host interface. This Application note helps to easily design antennas for NTAG 5 switch and NTAG 5 link (passive load modulation).

## 2. Antenna theory

### 2.1 NTAG 5 switch and NTAG 5 link connections

The NTAG 5 needs to be connected to the antenna with the pads  $L_A$  and  $L_B$

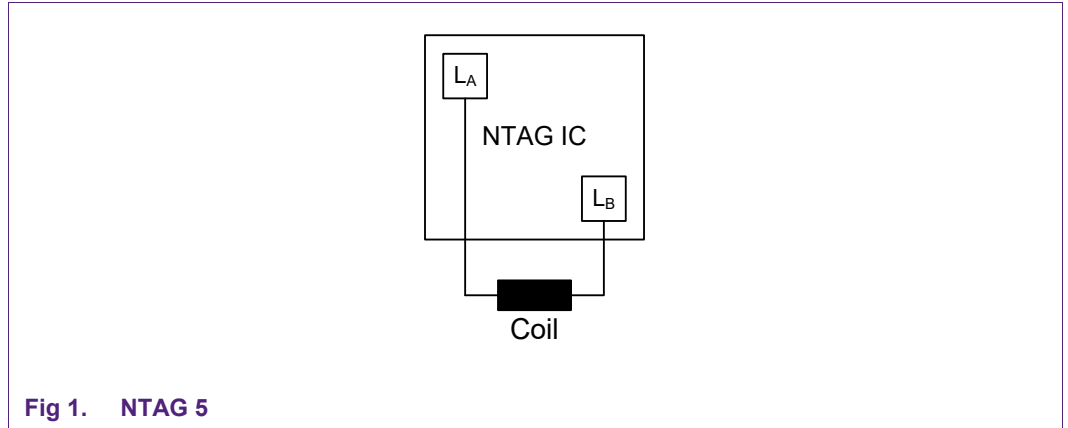


Fig 1. NTAG 5

#### 2.1.1 NTAG 5 IC equivalent circuit

The following simple equivalent circuit describes the properties of the NTAG 5 which are relevant for the antenna design.

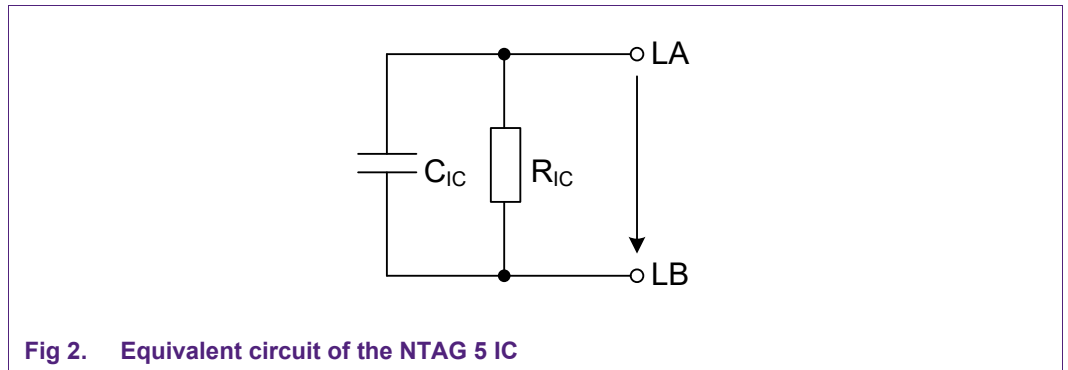


Fig 2. Equivalent circuit of the NTAG 5 IC

#### 2.1.2 NTAG 5 input capacitance $C_{IC}$

This electrical parameter of the NTAG 5 IC is the most important factor for the antenna design. The form factor and the parameters of the antenna are affected by the input capacitance.

The input capacitance depends on the applied chip voltage. Because the antenna voltage is limited in the operational state which stabilize the input capacitance as well all further calculations should be done in the operational state. The effect of capacitance variations results in different measured resonance frequencies on the network analyzer.

The following table specifies the operational state values of this capacitance for the given type of NTAG 5 IC.


**Table 1. Capacitance value of NTAG 5 link and NTAG 5 switch**

Type	C <sub>ic</sub>	Measurement conditions
NTP5332, NTP5312, NTP5210	15pF	V <sub>LA-LB</sub> = 1.8Vp, Network Analyzer (f = 13.56 MHz) @ room temp.

## 2.2 Series and parallel equivalent circuits

### 2.2.1 Series equivalent circuit of the antenna

The antenna can be described by an inductance L<sub>sc</sub> in series to a loss resistance R<sub>sc</sub>. The antenna capacitance C<sub>c</sub> is in parallel to this series circuit. This capacitance consists of the inter-turn capacitance and a possibly designed tag capacitance C<sub>ic</sub>.

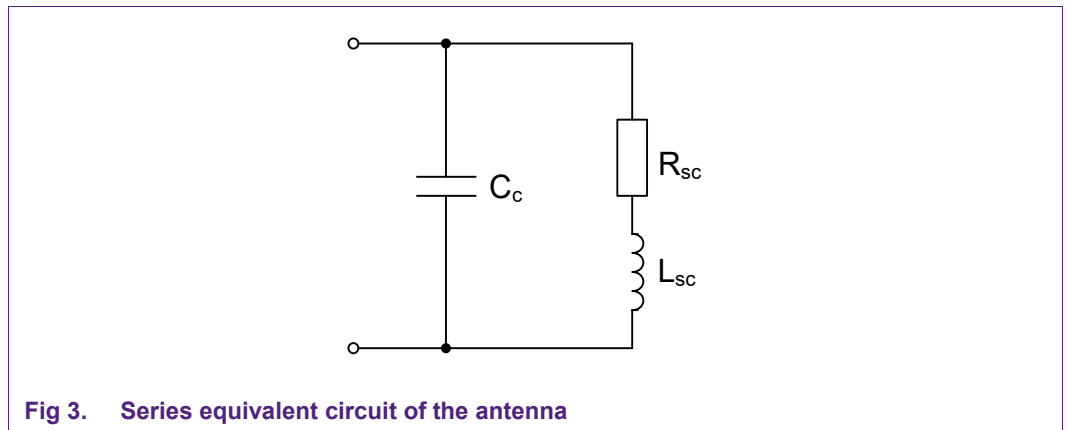

**Fig 3. Series equivalent circuit of the antenna**

The antenna quality factor is calculated by

$$Q_{sc} = \frac{2 \cdot \pi \cdot f_{op} \cdot L_{sc}}{R_{sc}}$$

with operating frequency  $f_{op} = 13.56$  MHz.

2.2.2 Parallel equivalent circuit of the antenna

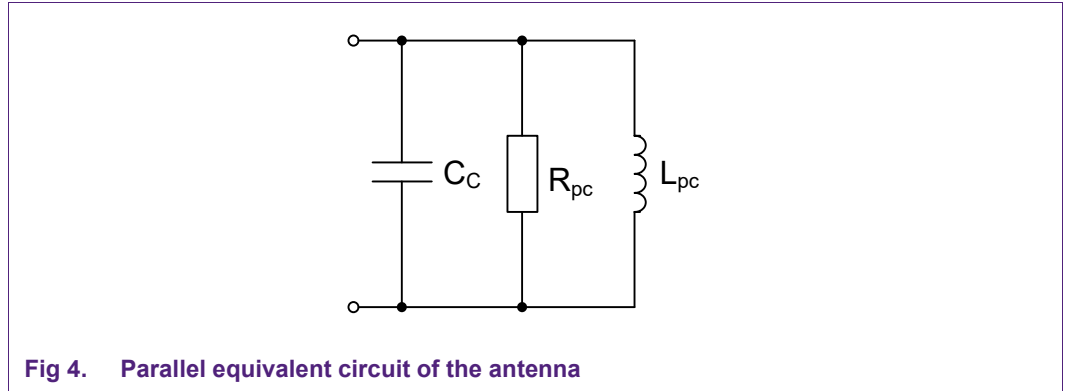


Fig 4. Parallel equivalent circuit of the antenna

The following applies:

$$L_{pc} = \frac{R_{sc}^2 + (2 \cdot \pi \cdot f_{op} \cdot L_{sc})^2}{(2 \cdot \pi \cdot f_{op})^2 \cdot L_{sc}} = L_{sc} \cdot \frac{1 + Q_{sc}^2}{Q_{sc}^2}$$

$$R_{pc} = \frac{R_{sc}^2 + (2 \cdot \pi \cdot f_{op} \cdot L_{sc})^2}{R_{sc}} = R_{sc} \cdot (1 + Q_{sc}^2)$$

$$Q_{pc} = \frac{R_{pc}}{2 \cdot \pi \cdot f_{op} \cdot L_{pc}} = Q_{sc}$$

For the further calculations, the parallel equivalent circuit was chosen to simplify the resonance circuit. This makes calculation easier.

2.2.3 Equivalent circuit of the tag

The following figure shows the equivalent circuit of the whole tag.

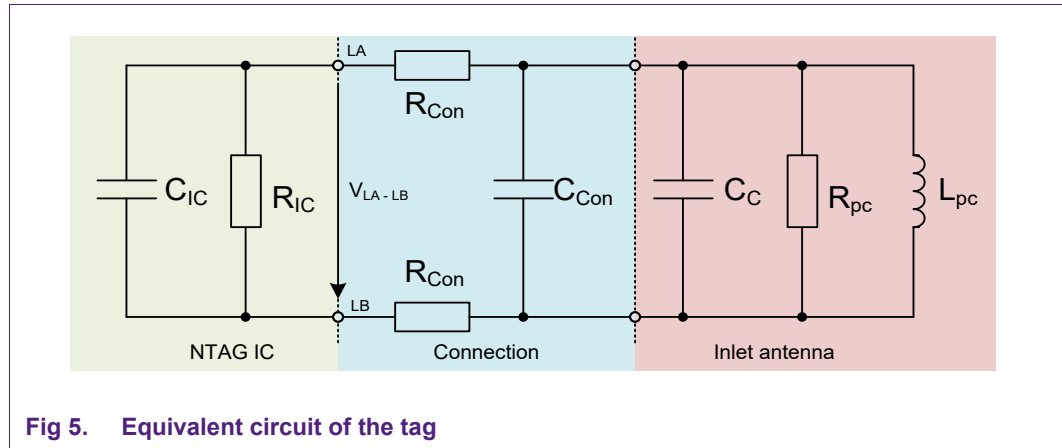


Fig 5. Equivalent circuit of the tag

The NTAG 5 IC capacitance  $C_{IC}$  together with the antenna capacitance and the parasitic connection capacitance forms a resonance circuit with the inductance of the antenna.

The NTAG 5 IC input resistance  $R_{IC}$  together with the loss resistance of the antenna and the connection resistance defines the quality factor of the tag when it is on its threshold power-on level. This quality factor influences the threshold field strength of the tag and will be explained in the following sections.

$R_{Con}$  should be kept as low as possible in order not to influence the total parallel equivalent resistance of the tag  $R_{pl}$ . A relatively high connection resistance will decrease the total parallel quality factor of the tag and therefore decrease the transmission range.

$C_{Con}$  describes the increase of the total tag capacitance due to dielectric changes (under filler, adhesive ...) in the connection area when the chip is applied to the antenna.

For  $R_{Con} \ll 1\Omega$  the following simplified circuit can be used for the IC:

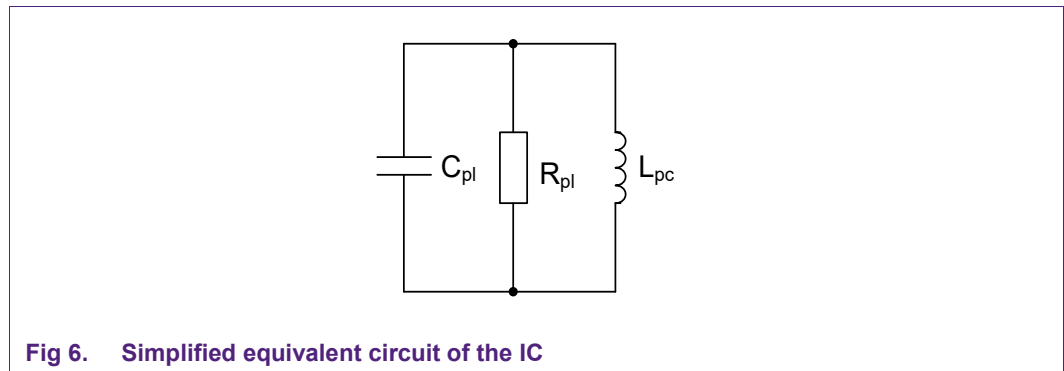


Fig 6. Simplified equivalent circuit of the IC

Parallel equivalent capacitance of the IC

$$C_{pl} = C_{IC} + C_{Con} + C_c$$

Parallel equivalent resistance of the tag

$$R_{pl} = \frac{R_{IC} \cdot R_{pc}}{R_{IC} + R_{pc}}$$

## 2.3 Resonance frequency and quality factor of the IC

Based on the simplified equivalent circuit the resonance frequency  $f_R$  of the IC can be calculated with:

$$f_R = \frac{1}{2 \cdot \pi \cdot \sqrt{L_{pc} \cdot C_{pl}}}$$

The value of the NTAG 5 IC input capacitance  $C_{IC}$  depends on the chip input voltage  $V_{LA-LB}$ . Therefore, the resonance frequency of the tag changes with the IC input voltage.

Based on the simplified equivalent circuit (Fig 6) the quality factor  $Q$  of the IC at the operating frequency can be calculated with:

$$Q = \frac{R_{pl}}{2 \cdot \pi \cdot f_{op} \cdot L_{pc}}$$

The value of the NTAG 5 IC input resistance  $R_{IC}$  depends on the chip input voltage  $V_{LA-LB}$ . Therefore, also the quality factor of the IC changes with the input voltage.

### 2.3.1 Threshold resonance frequency $f_{RT}$ and threshold quality factor $Q_T$

The threshold resonance frequency  $f_{RT}$  is the resulting resonance frequency for the minimum operating input voltage of the IC.

$V_{LA-LB}$  Minimal voltage level for NTAG 5 IC operation

$$C_{plT} = C_{ICT} + C_{Con} + C_c$$

$C_{ICT}$  NTAG 5 IC input capacitance for threshold condition

$C_{plT}$  Parallel equivalent capacitance of the IC for threshold condition

$C_{ICT}$  represents the NTAG 5 IC input capacitance for minimal operating conditions and corresponds to the specified typical value.

$$f_{RT} = \frac{1}{2 \cdot \pi \cdot \sqrt{L_{pc} \cdot C_{plT}}}$$

$$R_{plT} = \frac{R_{ICT} \cdot R_{pc}}{R_{ICT} + R_{pc}}$$



$R_{ICT}$  NTAG 5 IC input resistance for threshold condition

$R_{pIT}$  Parallel equivalent resistance of the IC for threshold condition

$R_{ICT}$  represents the NTAG 5 IC input resistance for the minimal operating conditions and corresponds to the shown typical value.

$$Q_T = \frac{R_{pIT}}{2 \cdot \pi \cdot f_{RT} \cdot L_{pc}}$$

## 2.4 Threshold field strength $H_T$ in passive communication mode

This section gives formulas to calculate the threshold field strength  $H_T$  which is significant for the transmission range. The influence of the threshold resonance frequency  $f_{RT}$  and the antenna quality factor  $Q_{pc}$  on this field strength is figured out.

To calculate the Voltage the mutual inductance needs to be calculated. The mutual inductance depends on the coupling between the Tag antenna and the reader antenna and can be calculated as:

$$M = k \cdot \sqrt{L1 \cdot L2}$$


The voltage on the IC generated by the magnetic field of the reader with antenna current  $I_1$  is given by:

$$V_{LA-LB} = \frac{2 \cdot \pi \cdot f \cdot M}{\left( \left( 1 - \left( \frac{f}{f_R} \right)^2 \right)^2 + \left( \frac{2 \cdot \pi \cdot f \cdot L_{pc}}{R_{pl}} \right)^2 \right)^{1/2}} \cdot I_1$$

With the assumption that the turns of the tag antenna are concentrated on the average antenna dimensions, the threshold field strength for NTAG 5 IC operation can be calculated with:

$$H_T = \frac{\left( \left( 1 - \left( \frac{f}{f_{RT}} \right)^2 \right)^2 + \left( \frac{2 \cdot \pi \cdot f \cdot L_{pc}}{R_{plT}} \right)^2 \right)^{1/2}}{2 \cdot \pi \cdot f \cdot \mu_0 \cdot N_c \cdot A_c} \cdot V_{LA-LB \min}$$

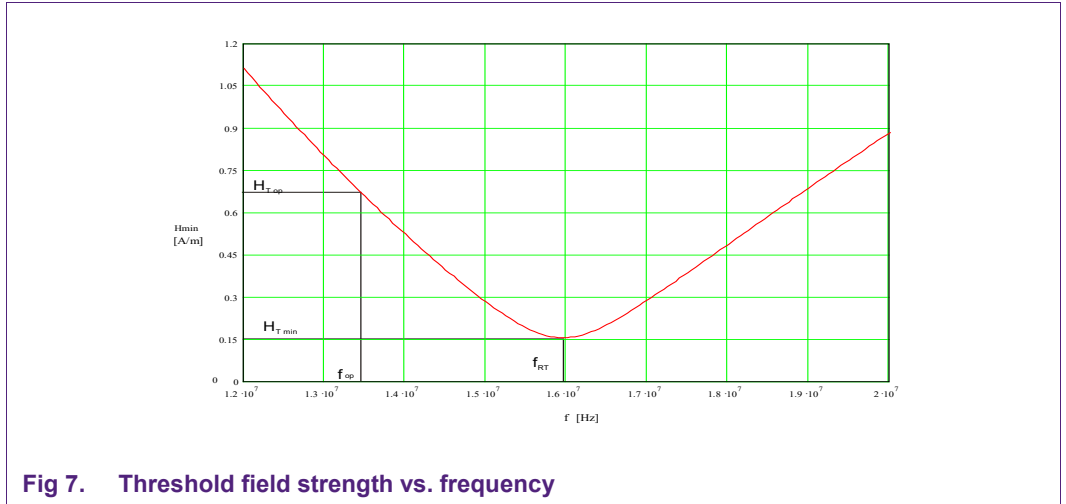The following figure shows the behavior of threshold field strength  $H_T$  versus the frequency  $f$  of the inducing magnetic field for a tag with the threshold resonance frequency  $f_{RT}$ .



The curve of the threshold field strength reaches its minimum at the threshold resonance frequency  $f_{RT}$  of the tag. For  $f=f_{RT}$  the minimal threshold field strength  $H_{Tmin}$  results in:

$$H_{Tmin} = \frac{L_{pc}}{\mu_0 \cdot N_c \cdot A_c \cdot R_{pIT}} \cdot V_{LA-LBmin}$$

At the operating frequency  $f_{op}$  the threshold field strength results in:


$$H_{Top} = \frac{\left( \left( 1 - \left( \frac{f_{op}}{f_{RT}} \right)^2 \right)^2 + \left( \frac{2 \cdot \pi \cdot f_{op} \cdot L_{pc}}{R_{pIT}} \right)^2 \right)^{1/2}}{2 \cdot \pi \cdot \mu_0 \cdot f_{op} \cdot N_c \cdot A_c} \cdot V_{LA-LBmin}$$

Lowest operating field strength is reached if  $f_{RT} = f_{op} = 13.56$  MHz resulting in  $H_T = H_{Tmin}$ .

### 3. Antenna matching

NTAG 5 link/switch with passive load modulation (PLM) is targeted for antennas bigger class 6.

#### 3.1 PLM topology

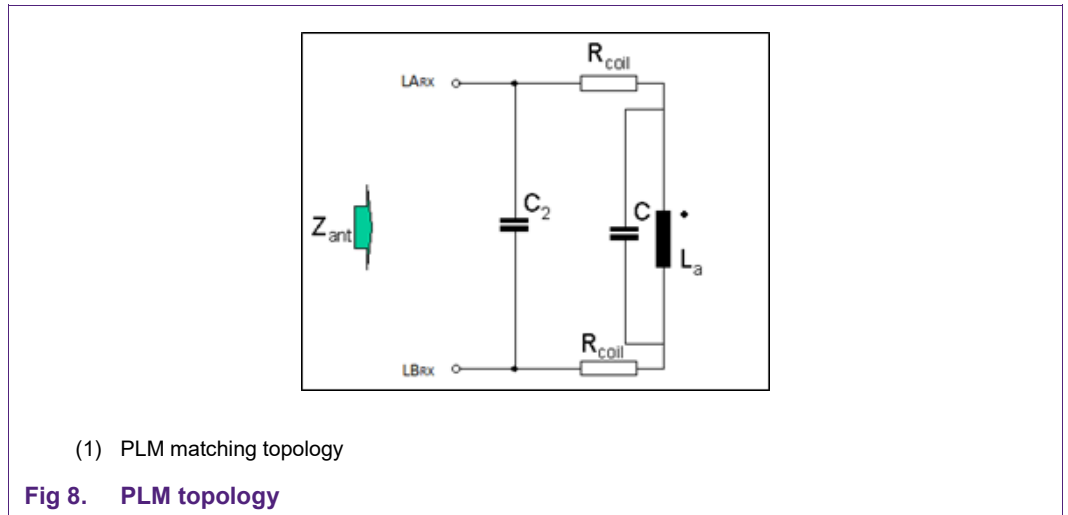

#### 3.2 General antenna matching procedure and preparation ALM and PLM

For a proper antenna design the antenna impedance must be measured using an impedance analyzer or VNA (vector network analyzer). Such a VNA can be a high-end tool from Agilent or Rohde & Schwarz (like the R&S ZVL), as normally used in this document), but might be a cheap alternative with less accuracy like e.g. the miniVNA Pro (see). In any case the analyzer needs to be able to measure the impedance in magnitude and phase (vector).

Such VNA can be used to measure the antenna coil as well as the antenna impedance including the matching circuit.

The antenna matching is done with the following steps:

1. Measure the antenna coil
2. Calculate the matching components
3. Simulate the matching
4. Assembly and measurement
5. Adaptation of simulation
6. Correction and assembly


3.2.1 Measure the antenna coil



The antenna coil must be designed as described in [section 2 Antenna theory](#) and be measured. The measurement is required to derive the inductance L, the resistance R<sub>Coil</sub> and the capacitance C<sub>pa</sub> as accurate as possible.

The easiest even though not most accurate way is to use the VNA to measure the impedance  $\underline{Z}$  of the antenna coil at 13.56MHz and to calculate L and R out of it:

$$\underline{Z} = R + j\omega L_{Coil} \tag{1}$$

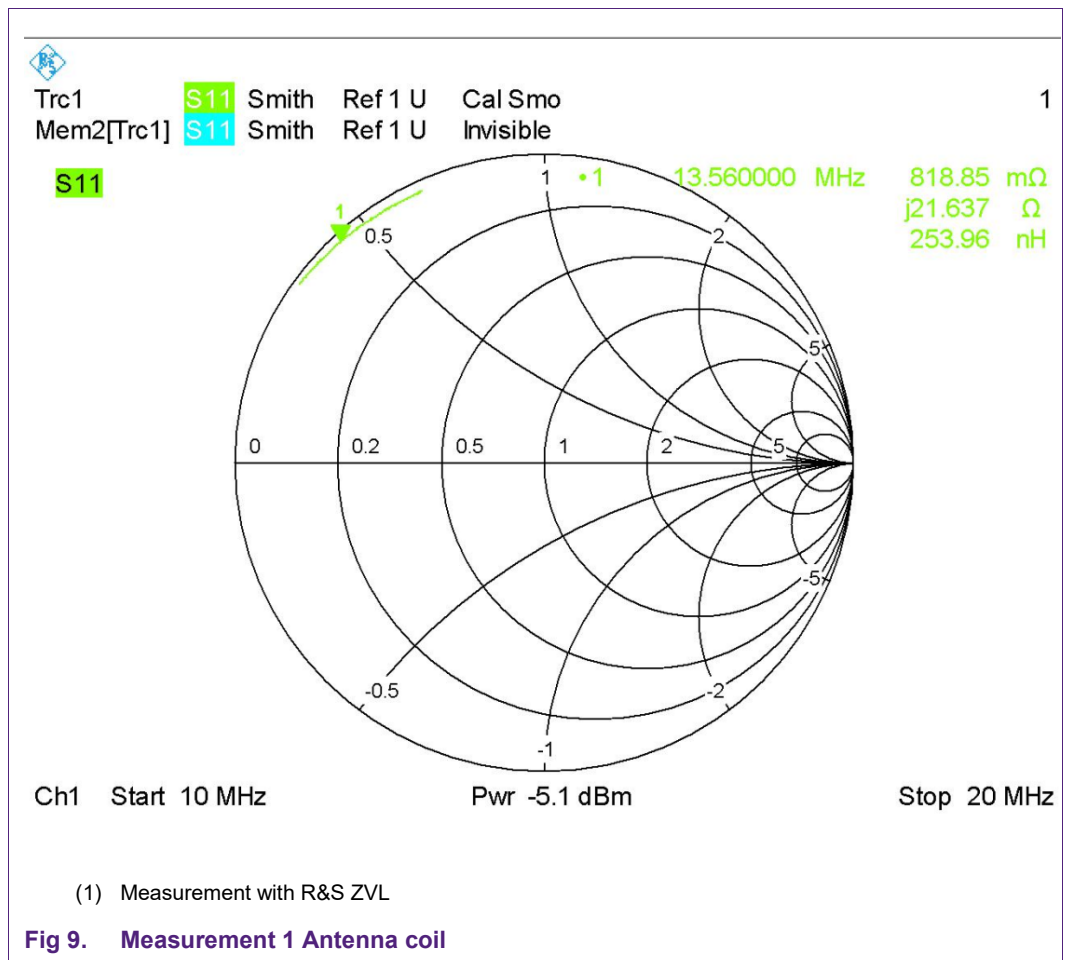Typically the VNA directly can show the L and R, as shown in Fig 9 and Fig 10.



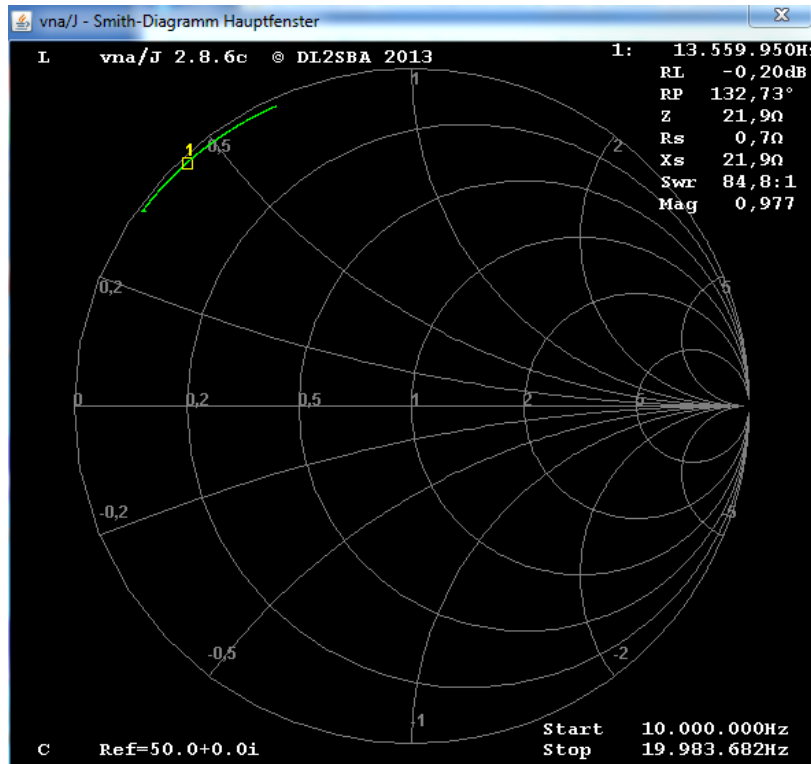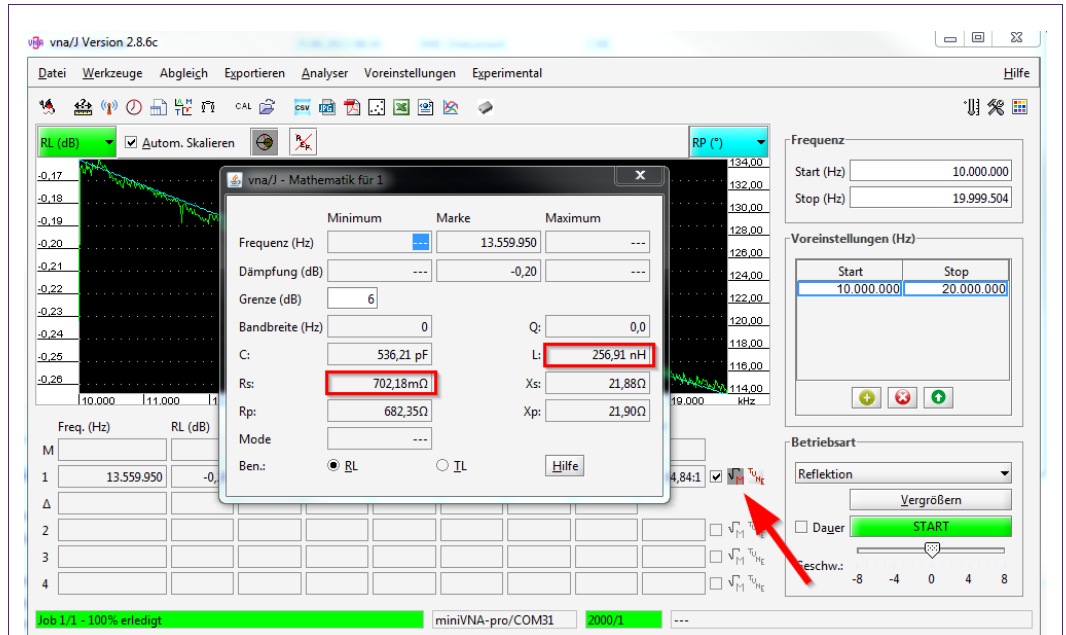

(2) Measurement with miniVNA Pro and vna/J

Fig 10. Measurement 2 Antenna coil

In this example the antenna coil is measured with these values:

$$L = 253\text{nH}$$

$$R_{\text{Coil}} = 0,7 \dots 0,82\Omega$$

$$C_{\text{pa}} = \text{not measured, can be estimated (typical in the range of 1-8pF)}$$

The inductance can be measured quite accurate, but the resistance is not very accurate due to the relationship between R and  $j\omega L$ . And the capacitance is not measured at all with this simple measurement.

There are several ways to improve the accuracy and even further derive the capacitance, but these simple results are enough to start the tuning procedure. This tuning procedure needs to be done anyway, so there is no real need to spend more effort in measuring the antenna coil parameters more accurate.

### 3.3 PLM matching

The next step is to calculate the values of the matching circuit.

To generate the matching values the measured antenna values must be inserted in the calculation sheet (see 0 ):

#### 3.3.1 PLM antenna measurement and matching calculation

##### 1 Measured" values:

$$L_a = L = 250\text{nH (measured antenna coil inductance)}$$

$$C_a = C_{\text{pa}} = 0.1\text{pF (estimated parallel capacitance of the antenna coil)}$$


Additional to the measured values, the target values for must be added.

##### 2 Preset values:

$$f_{\text{target}} = 13,56\text{MHz}$$
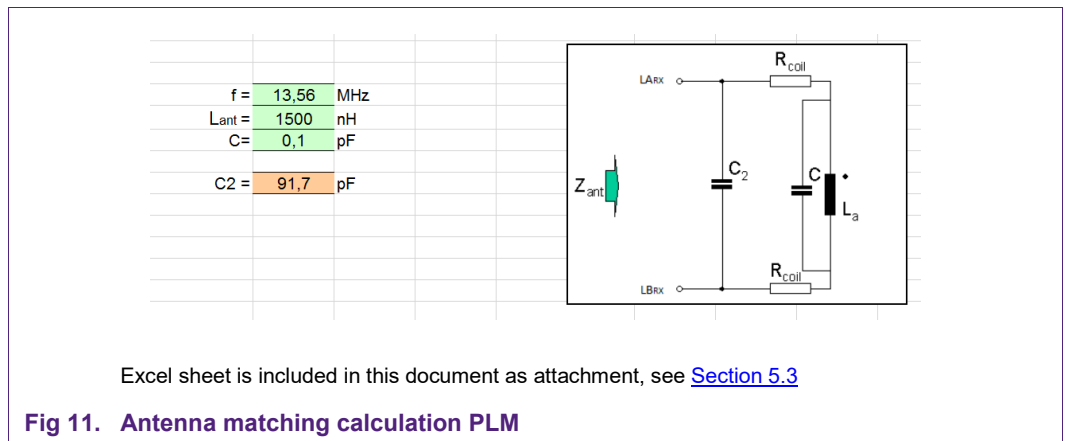
##### 3 Calculated Values and components: [\(Fig 11\)](#)

$$C_2 = 91,7\text{pF} \quad \rightarrow 82\text{pF} + 10\text{pF (0,3pF additional)}$$




### 3.3.2 Simulate the matching

The measurement of the antenna coil itself typically is not very accurate, except the inductance. Therefore a (fine) tuning of the antenna can be required, which might become easier in combination together with a simulation.

A simple matching simulation tool like e.g. RFSIM99 can be used to support the antenna tuning. The simulation input and the result based on the above given start values for the antenna matching is shown in

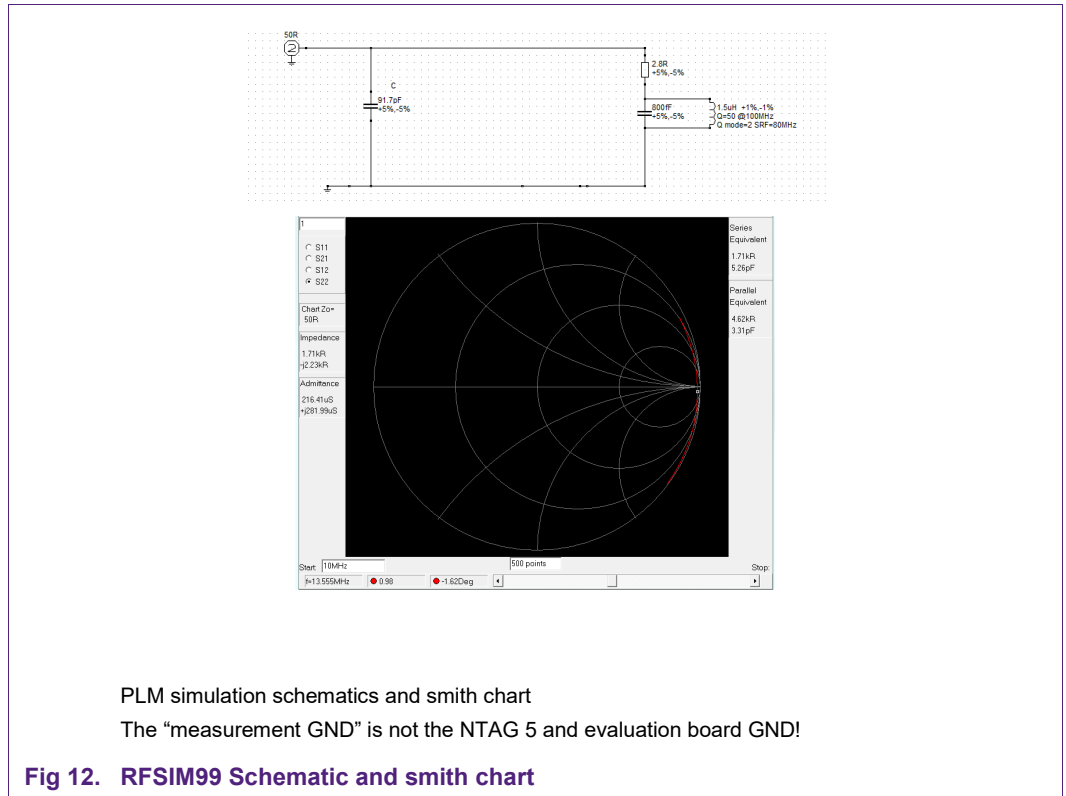With these values the assembly can be done,





## 4. List of abbreviations

This document uses the following list of abbreviations:

$A_c$	Average antenna area
$A_{Active}$	Active antenna area
$A_i$	Area of antenna winding $i$
$a_{avg}, b_{avg}$	Average dimensions of the antenna
$a_{max}, b_{max}$	Maximum dimensions of the antenna
$a_o, b_o$	Overall dimensions of the antenna
$C_c$	Antenna capacitance
$C_{br}$	Bridge capacitance
$C_{Con}$	Capacitance due the connection NTAG 5 IC – antenna
$C_{IC}$	NTAG 5 IC input capacitance
$C_{ICT}$	NTAG 5 IC input capacitance for threshold condition
$C_{in}$	Designed inlet capacitance
$C_{it}$	Inter turn capacitance of the antenna
$C_{pl}$	Parallel equivalent capacitance of the inlet
$C_{plT}$	Parallel equivalent capacitance of the inlet for threshold condition
$d$	Antenna wire diameter
$f$	Frequency
$f_{op}$	Operating frequency
$f_R$	Resonance frequency of the inlet
$f_{RT}$	Threshold resonance frequency of the inlet
$g$	Gap between the tracks
$H_T$	Threshold field strength
$H_{Tmin}$	Minimal threshold field strength
$H_{Top}$	Threshold field strength at operating frequency
$I_1$	Reader antenna current
$L_{calc}$	Inductance calculated out of the geometrical antenna parameters
$L_o$	Objective inductance of the antenna
$L_{pc}$	Parallel equivalent inductance of the antenna
$L_{sc}$	Serial equivalent inductance of the antenna
$M$	Mutual inductance between the inlet antenna and reader antenna
$N_c$	Number of turns of the antenna
$p$	Turn exponent
$Q$	Quality factor of the inlet
$Q_{pc}$	Quality factor of the antenna for parallel equivalent circuit
$Q_{sc}$	Quality factor of the antenna for serial equivalent circuit
$Q_T$	Threshold quality factor of the inlet
$R_{Con}$	Resistance of the connection NTAG 5 IC – antenna

$R_{IC}$	NTAG 5 IC input resistance
$R_{ICT}$	NTAG 5 IC input resistance for threshold condition
$R_{pc}$	Parallel equivalent resistance of the antenna
$R_{pl}$	Parallel equivalent resistance of the inlet
$R_{plT}$	Parallel equivalent resistance of the inlet at threshold condition
$R_{sc}$	Serial equivalent resistance of the antenna
$t$	Track thickness
$V_{LA-LB}$	NTAG 5 IC input voltage
$V_{LA-LB \text{ min}}$	Minimal voltage level for NTAG 5 IC operation
$w$	Track width

## 5. Reference documentation

---

NXP provides several documents to support the development of customized antennas.

### 5.1 Data sheets

NXP provides the following datasheets:

- NTP5210 - NTAG 5 switch, NFC Forum-compliant PWM and GPIO bridge, Product data sheet, doc.no. 544630  
<https://www.nxp.com/docs/en/data-sheet/NTP5210.pdf>
- NTP53x2 - NTAG 5 link, NFC Forum-compliant I2C bridge, Product data sheet, doc.no. 544530  
<https://www.nxp.com/docs/en/data-sheet/NTP53x2.pdf>

### 5.2 Application notes

NXP provides the following application note:

- AN12428 - NTAG 5 design recommendations for FCC and CE certifications  
<https://www.nxp.com/docs/en/application-note/AN12428.pdf>

### 5.3 Included antenna matching calculation excel sheet

As attachment you will find a ZIP file containing the antenna matching calculator.

The Excel file is enclosed in a ZIP file which has the file extension .nxp. To access the Excel file, you can do the following:

- Open the attachment by clicking the paperclip in the left margin.
- You will find a .nxp file added to this PDF as an attachment. Right-click the file and click Save Attachment. Store it at a permanently available (network) storage location.
- Open the location where you saved the attachment.
- Rename the file. Change the extension from .nxp into .zip.
- Now you can open the zip file which contains the Excel file.

## 6. Legal information

### 6.1 Definitions

**Draft** — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. NXP Semiconductors does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

### 6.2 Disclaimers

**Limited warranty and liability** — Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information.

In no event shall NXP Semiconductors be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, NXP Semiconductors' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the Terms and conditions of commercial sale of NXP Semiconductors.

**Right to make changes** — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

**Suitability for use** — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an NXP Semiconductors product can reasonably be expected to result in personal injury, death or severe property or environmental damage. NXP Semiconductors accepts no liability for inclusion and/or use of NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

**Applications** — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using NXP Semiconductors products, and NXP Semiconductors accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the NXP Semiconductors product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

NXP Semiconductors does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using NXP Semiconductors products in order to avoid a default of the applications and

the products or of the application or use by customer's third party customer(s). NXP does not accept any liability in this respect.

**Export control** — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from competent authorities.

**Evaluation products** — This product is provided on an "as is" and "with all faults" basis for evaluation purposes only. NXP Semiconductors, its affiliates and their suppliers expressly disclaim all warranties, whether express, implied or statutory, including but not limited to the implied warranties of non-infringement, merchantability and fitness for a particular purpose. The entire risk as to the quality, or arising out of the use or performance, of this product remains with customer.

In no event shall NXP Semiconductors, its affiliates or their suppliers be liable to customer for any special, indirect, consequential, punitive or incidental damages (including without limitation damages for loss of business, business interruption, loss of use, loss of data or information, and the like) arising out of the use of or inability to use the product, whether or not based on tort (including negligence), strict liability, breach of contract, breach of warranty or any other theory, even if advised of the possibility of such damages.

Notwithstanding any damages that customer might incur for any reason whatsoever (including without limitation, all damages referenced above and all direct or general damages), the entire liability of NXP Semiconductors, its affiliates and their suppliers and customer's exclusive remedy for all of the foregoing shall be limited to actual damages incurred by customer based on reasonable reliance up to the greater of the amount actually paid by customer for the product or five dollars (US\$5.00). The foregoing limitations, exclusions and disclaimers shall apply to the maximum extent permitted by applicable law, even if any remedy fails of its essential purpose.

### 6.3 Licenses

#### Purchase of NXP ICs with NFC technology

Purchase of an NXP Semiconductors IC that complies with one of the Near Field Communication (NFC) standards ISO/IEC 18092 and ISO/IEC 21481 does not convey an implied license under any patent right infringed by implementation of any of those standards. Purchase of NXP Semiconductors IC does not include a license to any NXP patent (or other IP right) covering combinations of those products with other products, whether hardware or software.

### 6.4 Trademarks

Notice: All referenced brands, product names, service names and trademarks are property of their respective owners.

**NTAG** — is a trademark of NXP B.V.

**PC-bus** — logo is a trademark of NXP B.V.

**AMBA, Arm, Arm7, Arm7TDMI, Arm9, Arm11, Artisan, big.LITTLE, Cordio, CoreLink, CoreSight, Cortex, DesignStart, DynamIQ, Jazelle, Keil, Mali, Mbed, Mbed Enabled, NEON, POP, RealView, SecurCore, Socrates, Thumb, TrustZone, ULINK, ULINK2, ULINK-ME, ULINK-PLUS, ULINKpro, µVision, Versatile** — are trademarks or registered trademarks of Arm Limited (or its subsidiaries) in the US and/or elsewhere. The related technology may be protected by any or all of patents, copyrights, designs and trade secrets. All rights reserved.

## 7. List of figures

---

Fig 1.	NTAG 5.....	4
Fig 2.	Equivalent circuit of the NTAG 5 IC .....	4
Fig 3.	Series equivalent circuit of the antenna .....	5
Fig 4.	Parallel equivalent circuit of the antenna .....	6
Fig 5.	Equivalent circuit of the tag .....	7
Fig 6.	Simplified equivalent circuit of the IC .....	7
Fig 7.	Threshold field strength vs. frequency .....	11
Fig 8.	PLM topology .....	12
Fig 9.	Measurement 1 Antenna coil .....	13
Fig 10.	Measurement 2 Antenna coil .....	14
Fig 11.	Antenna matching calculation PLM.....	16
Fig 12.	RFSIM99 Schematic and smith chart.....	17

## 8. List of tables

---

Table 1. Capacitance value of NTAG 5 link and NTAG 5 switch.....5

## 9. Contents

<b>1.</b>	<b>Introduction .....</b>	<b>3</b>
<b>2.</b>	<b>Antenna theory .....</b>	<b>4</b>
2.1	NTAG 5 switch and NTAG 5 link connections....	4
2.1.1	NTAG 5 IC equivalent circuit.....	4
2.1.2	NTAG 5 input capacitance $C_{IC}$ .....	4
2.2	Series and parallel equivalent circuits.....	5
2.2.1	Series equivalent circuit of the antenna .....	5
2.2.2	The antenna can be described by an inductance $L_{sc}$ in series to a loss resistance $R_{sc}$ . The antenna capacitance $C_c$ is in parallel to this series circuit. This capacitance consists of the inter-turn capacitance and a possibly designed tag capacitance $C_{IC}$ .....	5
2.2.3	Parallel equivalent circuit of the antenna.....	6
2.2.4	Equivalent circuit of the tag .....	7
2.3	Resonance frequency and quality factor of the IC .....	8
2.3.1	Threshold resonance frequency $f_{RT}$ and threshold quality factor $Q_T$ .....	8
2.4	Threshold field strength $H_T$ in passive communication mode .....	10
<b>3.</b>	<b>Antenna matching .....</b>	<b>12</b>
3.1	PLM topology .....	12
3.2	General antenna matching procedure and preparation ALM and PLM .....	12
3.2.1	Measure the antenna coil.....	13
3.3	PLM matching .....	15
3.3.1	PLM antenna measurement and matching calculation .....	15
3.3.2	Simulate the matching.....	16
<b>4.</b>	<b>List of abbreviations .....</b>	<b>18</b>
<b>5.</b>	<b>Reference documentation .....</b>	<b>20</b>
5.1	Data sheets .....	20
5.2	Application notes.....	20
5.3	ISO/IEC standards .....	20
<b>6.</b>	<b>Legal information .....</b>	<b>21</b>
6.1	Definitions .....	21
6.2	Disclaimers.....	21
6.3	Licenses.....	21
6.4	Trademarks.....	21
<b>7.</b>	<b>List of figures.....</b>	<b>22</b>
<b>8.</b>	<b>List of tables .....</b>	<b>23</b>
<b>9.</b>	<b>Contents.....</b>	<b>24</b>