

AN1775

Expanding Digital Input with an A/D Converter

By Brad Bierschenk
Freescale Applications Engineering
Austin, Texas

Introduction

This application note documents a method of extending digital input using the analog-to-digital converter (ADC) of a microcontroller unit (MCU).

Many MCU applications require digital input and arbitration. For example, determining which key of a keypad was pressed. This is commonly done by arranging switches in a matrix configuration, connecting to a series of digital input pins, and reading a digital input data register to determine which key was pressed. While this method is easily implemented, it does require the use of an MCU's parallel port pins.

Some applications require all available bidirectional or input-only pins for other purposes. In such a case, an alternate method of arbitrating keypresses is desired. By using the ADC of an MCU connected to a resistor ladder, user input can be more efficiently processed.



Background

Dedicated Input A microcontroller typically receives user input through digital input pins. The simplest implementation is a single switch directly connected to a digital input pin. This is easy to realize, but is not the most efficient use of resources, with one pin dedicated to one input. One port data bit represents the state of one switch.

Matrix Input Another method uses a keypad, a common element in embedded systems. These are ordinarily arranged in a matrix, as shown in **Figure 1**. In this case, the byte value of an entire port data register can be polled to determine which key was pressed. This is more efficient, as a 4 x 4 keypad can interface 16 keys with eight input pins.

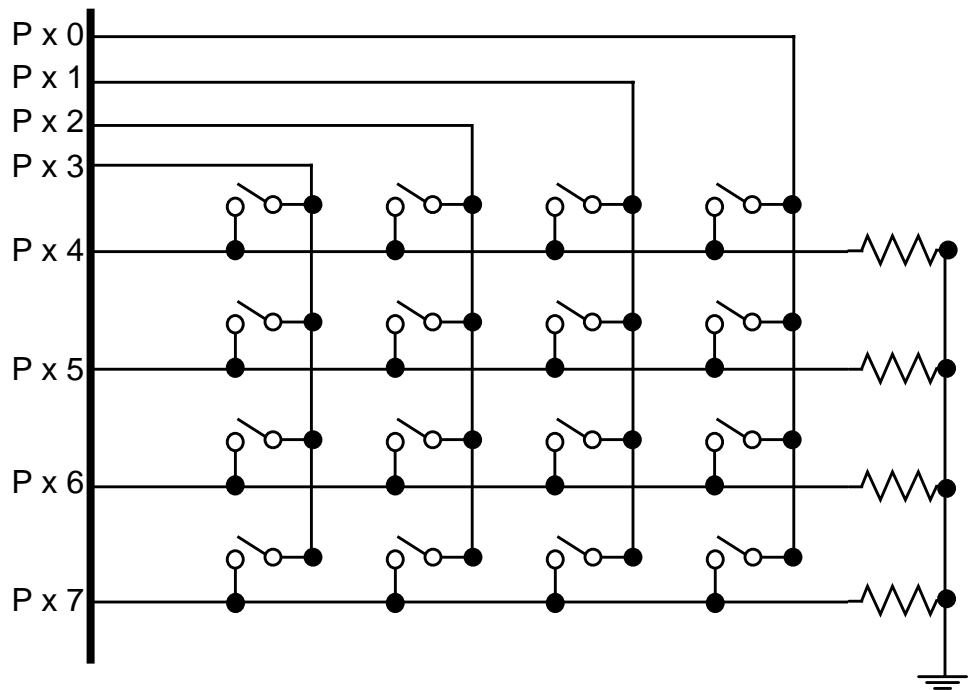


Figure 1. Resistor Matrix Keypad Using Parallel Port Pins

ADC Alternative

In many cases, input pins are at a premium. One can't always freely assign input pins to the function of user input. A more efficient use of microcontroller resources can be devised. One common feature of many Freescale MCUs is the analog-to-digital converter, or ADC.

The ADC of a Freescale MCU usually features four to eight channels of analog input, which is compared with a reference voltage and converted to an 8-bit digital value. When a resistor ladder is connected to an analog input through switches in each segment, the conversion result can be used to arbitrate an input. This allows many keys to be interfaced with one input pin, with only a little more software overhead. **Figure 2** shows such an implementation.

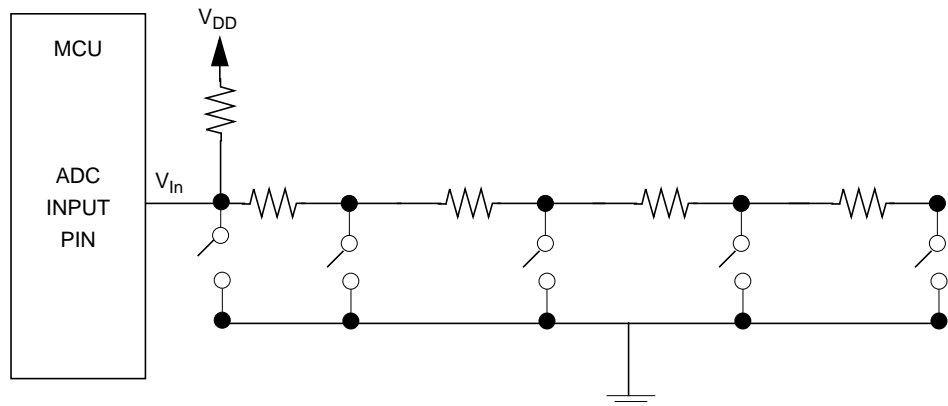


Figure 2. Resistor Ladder Keys Using an Analog Input Pin

Implementation

ADC Operation

An MCU ADC typically has 8-bit *precision*. This means there are 2^8 , or 256, distinguishable A/D inputs, including 0. The analog inputs are converted to a binary number, which represents the magnitude of the input voltage in relation to a reference voltage.

How to Reach Us:

Home Page:

www.freescale.com

E-mail:

support@freescale.com

USA/Europe or Locations Not Listed:

Freescale Semiconductor
Technical Information Center, CH370
1300 N. Alma School Road
Chandler, Arizona 85224
+1-800-521-6274 or +1-480-768-2130
support@freescale.com

Europe, Middle East, and Africa:

Freescale Halbleiter Deutschland GmbH
Technical Information Center
Schatzbogen 7
81829 Muenchen, Germany
+44 1296 380 456 (English)
+46 8 52200080 (English)
+49 89 92103 559 (German)
+33 1 69 35 48 48 (French)
support@freescale.com

Japan:

Freescale Semiconductor Japan Ltd.
Headquarters
ARCO Tower 15F
1-8-1, Shimo-Meguro, Meguro-ku,
Tokyo 153-0064
Japan
0120 191014 or +81 3 5437 9125
support.japan@freescale.com

Asia/Pacific:

Freescale Semiconductor Hong Kong Ltd.
Technical Information Center
2 Dai King Street
Tai Po Industrial Estate
Tai Po, N.T., Hong Kong
+800 2666 8080
support.asia@freescale.com

For Literature Requests Only:

Freescale Semiconductor Literature Distribution Center
P.O. Box 5405
Denver, Colorado 80217
1-800-441-2447 or 303-675-2140
Fax: 303-675-2150
LDCForFreescaleSemiconductor@hibbertgroup.com

Information in this document is provided solely to enable system and software implementers to use Freescale Semiconductor products. There are no express or implied copyright licenses granted hereunder to design or fabricate any integrated circuits or integrated circuits based on the information in this document. Freescale Semiconductor reserves the right to make changes without further notice to any products herein. Freescale Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does Freescale Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation consequential or incidental damages. "Typical" parameters which may be provided in Freescale Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. Freescale Semiconductor does not convey any license under its patent rights nor the rights of others. Freescale Semiconductor products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the Freescale Semiconductor product could create a situation where personal injury or death may occur. Should Buyer purchase or use Freescale Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold Freescale Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that Freescale Semiconductor was negligent regarding the design or manufacture of the part.

